

## Lab 7 Instruction Fetch

### Lab 7 Objective:


To use our previous labs 4, 5 and 6 to be able to fully integrate the ALU, RAM, registers and data paths of the microprocessor. To understand exactly what this circuit does by creating a force file that will transfer and store data accordingly. Then to create a control unit that will provide the inputs to the controls of: the opcode, system flags, reset and the system clock.

### Activity 1: Hardware Design: Everything Except the Control Unit

#### Block Diagram:

The block diagram shown below is a combination of the code created from the previous labs. I altered the symbols for each file to match the given Block Diagram given in the Lab 7 PowerPoint. The code has also been modified in order to get all the control signals and data busses to communicate with each other. There are additional output pins to monitor their values while running the ModelSim Simulations.

#### bdf file

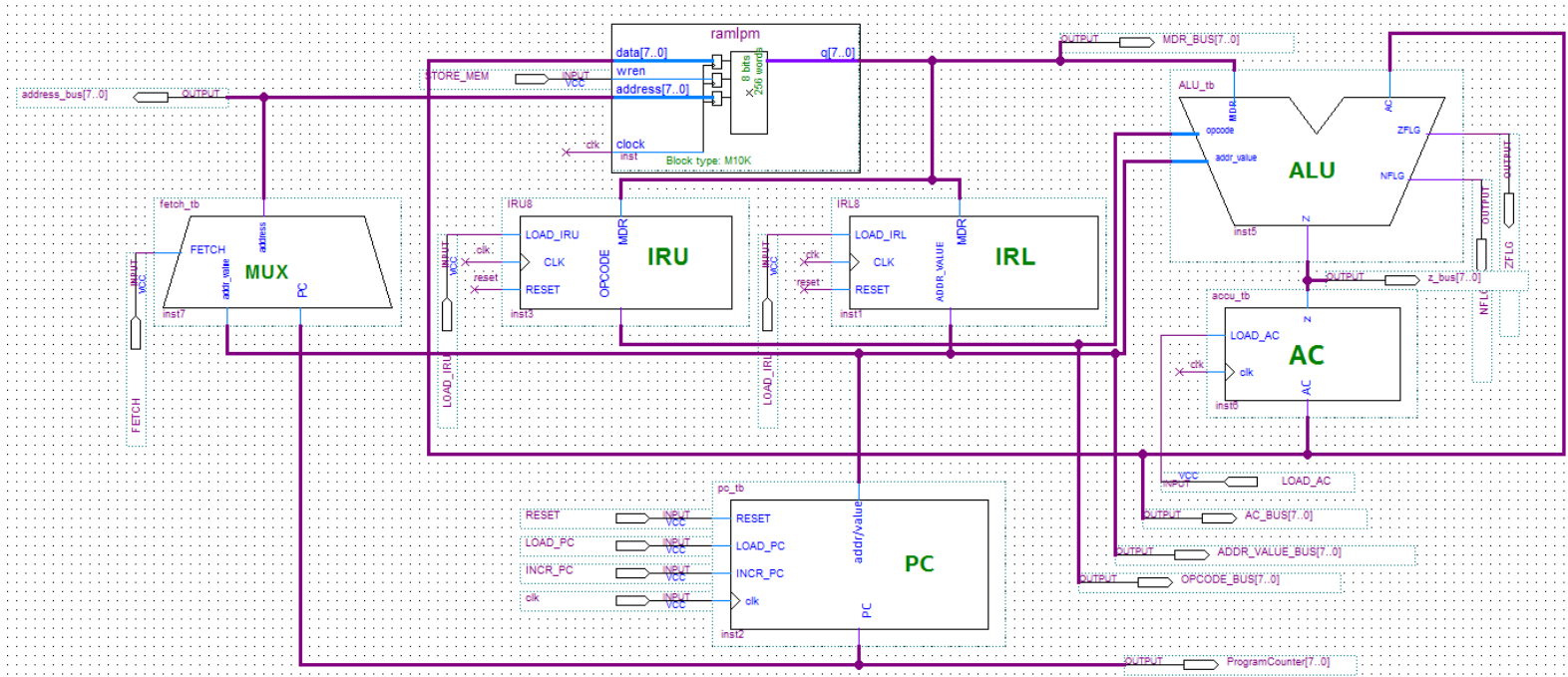

## Memory Initialization File

The first twelve memory locations x"00" to x"0B" were initialized to the hexadecimal values of 02, E7, 03, 10, 09, 10, 10, 0A, 0E, 03, 04, FF. For the Memory initialization file the values had to be converted into decimal representation as shown in the screenshot of the memory locations.

[illegible]

## Force File Act 1

```
#####
# EE310 Lab07 ACT1 Force File
# Demonstrate Control Signals
# Jessica Atkinson May 8, 2017
#####

# Restate Simulation when loaded
restart -force

# Reset and clear all registers
force RESET 1 0ns ;
force FETCH 0 0ns ;
force INCR_PC 0 0ns ;
force LOAD_PC 0 0ns;
force LOAD_IRL 0 0ns;
force LOAD_IRU 0 0ns;
force LOAD_AC 0 0ns;
force clk 0 0ns, 1 50ns -r 100ns;
force STORE_MEM 0 0ns;

# Run one clock cycle & turn off RESET
run 25ns;
force RESET 0 0ns;
run 75ns;

# Start repeat statements for the PrepU, FetchU, PrepL, FetchL state representations
# Made them repeat every 500ns (5 clock cycles)
force FETCH 1 0ns, 0 100ns, 1 200ns, 0 300ns -r 500ns;
force INCR_PC 0 0ns, 1 100ns, 0 200ns, 1 300ns, 0 400ns -r 500ns;
force LOAD_IRL 0 0ns, 1 300ns, 0 400ns -r 500ns;
force LOAD_IRU 0 0ns, 1 100ns, 0 200ns -r 500ns;

# From 400ns to 500ns of the repeat statements is when LOAD_AC, LOAD_PC and STORE_MEM will
# execute. Following statements are asserted from the given instructions.
run 400ns;

force LOAD_AC 1 0ns;
run 100ns;

force LOAD_AC 0 0ns;
run 400ns;

force STORE_MEM 1 0ns;
run 100ns;

force STORE_MEM 0 0ns;
run 400ns;

force LOAD_AC 1 0ns;
run 100ns;


force LOAD_AC 0 0ns;
run 400ns;

force LOAD_PC 1 0ns;
run 100ns;

force LOAD_PC 0 0ns;
run 400ns;
#####//end
```
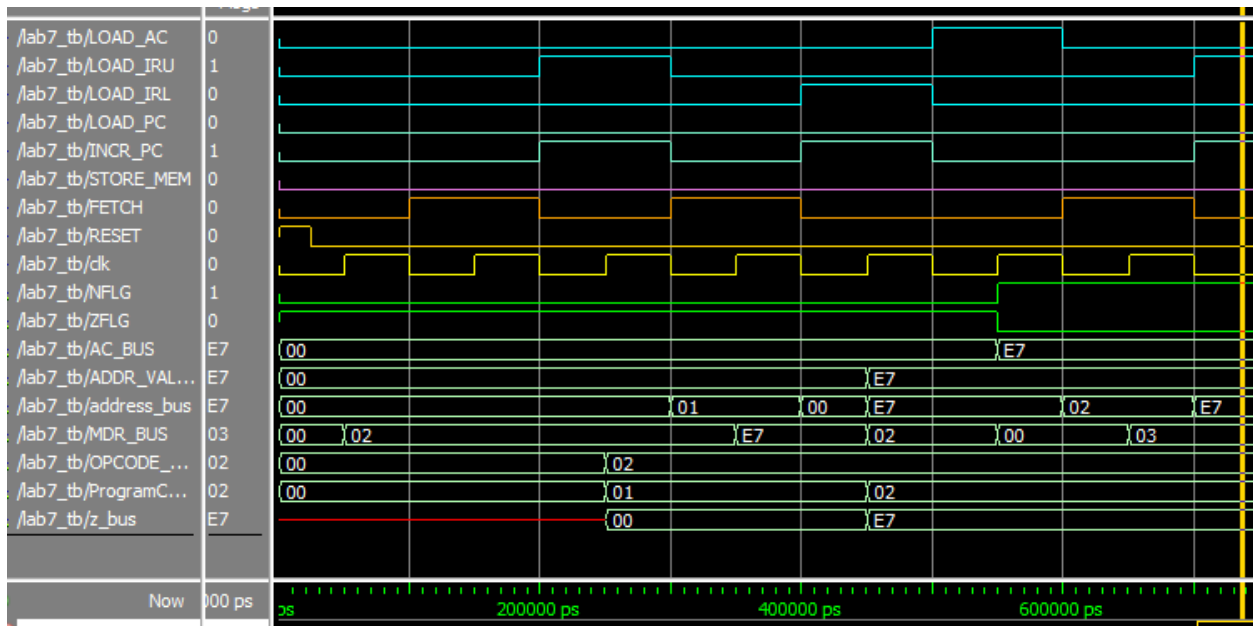
## Waveform


Below is the waveform produced from the compiled BDF and force file. I ran into some iteration issues at 750ns with an error. I've tried to determine the cause of this issue and couldn't seem to get rid of the error. For the first seven and a half clock cycles it appears that all the data is correctly being stored and transferred among the data busses on the RISING clock edge while the control lines only change on the FALLING clock edge giving the control signals and data busses 50ns to avoid timing issues.. ALU and FETCH are not controlled by the clock and update their data busses on both, rising and falling clock edges. I am not sure if this is what is causing the issue or if it is within the original code of the files.



## VHDL Code
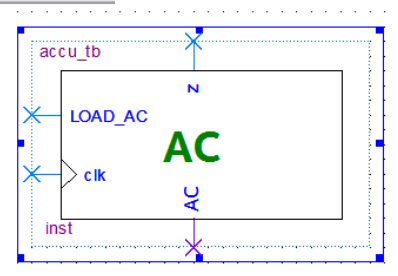
### Accumulator

```
1  --EE310 Lab07
2  --Accumulator
3
4
5
6  --import library
7  library ieee;
8  use ieee.std_logic_1164.all;
9
10 entity accu_tb is
11   port( z : in std_logic_vector(7 downto 0);
12         LOAD_AC, clk : in std_logic;
13         AC : out std_logic_vector(7 downto 0));
14 end entity accu_tb;
15
16 architecture behavior of accu_tb is
17 begin
18   process(z, clk, LOAD_AC) --sensitivity list
19   begin
20     IF LOAD_AC = '1' then --ELSIFF LOAD_AC (Sw8) is on
21       IF clk'event AND clk = '1' then --IF rising edge of clk
22         AC <= z; --store z bus data into the AC register
23       END IF;
24     END IF;
25   end process;
26 END behavior;
```




# ALU

## In the ALU

```

1  -- EE310 Lab05 ALU
2  -- Implements the instruction set
3  -- for the uP3 microprocessor in Lab 4
4
5
6  -- Author: Jessica Atkinson, NAU/CUPT EE
7
8
9  --declaring libraries used
10 library ieee;
11 use ieee.std_logic_1164.all;
12 use ieee.numeric_std.all;
13 library altera_mf;
14 use altera_mf.altera_mf_components.all;
15
16 --Entity
17 entity ALU_tb is
18 port(
19     AC_IN, MDR_IN, VALUE_IN, OPCODE_IN : in std_logic_vector(7 downto 0);
20     Z_OUT : out std_logic_vector(7 downto 0);
21     --LOAD_PC, STORE_MEM : out std_logic
22     ZFLG, NFLG : out std_logic;
23 );
24 end ALU_tb;
25
26 --architecture behavior of ALU_tb is
27 architecture behavior of ALU_tb is
28     SIGNAL OPCODE_REG, VALUE_OUT, AC_out, MDR_out : std_logic_vector(7 downto 0);
29     SIGNAL AC_SIGNED : signed(7 downto 0);
30     -- INSTRUCTION VARIABLES
31     SIGNAL Z, NOP, LOAD, LOADI, CLR, ADD, SUBT, NEG, NOT, ANDD, ORR, XOR, SHL, SHR : std_logic_vector(7 downto 0);
32     SIGNAL STORE, JUMP, JNEG, JPOSZ, JZERO, JNZER : std_logic;
33     signal ADDI, SUBTI : std_logic_vector(8 downto 0);
34     signal MEM_STORE, PC_LOAD : std_logic;
35
36 begin
37     --LOADING TMP REGISTER TO OUTPUTS
38     Z_OUT <= Z;
39     AC_OUT <= AC_IN;
40     MDR_OUT <= MDR_IN;
41     VALUE_OUT <= VALUE_IN;
42     OPCODE_REG <= OPCODE_IN;
43     AC_SIGNED <= signed(AC_IN);
44     STORE_MEM <= MEM_STORE;
45     LOAD_PC <= PC_LOAD;
46     ZFLG <= '1' WHEN (AC_IN = x"00") ELSE '0';
47     NFLG <= '1' WHEN (AC_SIGNED(7) = '1') ELSE '0';
48
49     -- CREATING THE INSTRUCTION SET
50     NOP <= Z;
51     LOAD <= MDR_IN;
52     LOADI <= VALUE_IN;
53     STORE <= '1';
54     CLR <= x"00";
55     ADD <= std_logic_vector(to_signed(to_integer(signed(AC_IN)) + to_integer(signed(MDR_IN)), 8));
56     ADDI <= std_logic_vector(('0' & unsigned(AC_IN)) + ('0' & unsigned(VALUE_IN)));
57     SUBT <= std_logic_vector(to_signed(to_integer(signed(AC_IN)) - to_integer(signed(MDR_IN)), 8));
58     SUBTI <= std_logic_vector(('0' & unsigned(AC_IN)) - ('0' & unsigned(VALUE_IN)));
59     NEG <= std_logic_vector(to_signed(to_integer(signed(CLR)) - to_integer(signed(MDR_IN)), 8));
60     NOT <= NOT MDR_IN;
61     ANDD <= (AC_IN AND MDR_IN);
62     ORR <= (AC_IN OR MDR_IN);
63     XOR <= (AC_IN XOR MDR_IN);
64     SHL <= std_logic_vector(unsigned(AC_IN) sll to_integer(unsigned(VALUE_IN(2 downto 0))));
65     SHR <= std_logic_vector(unsigned(AC_IN) srl to_integer(unsigned(VALUE_IN(2 downto 0))));
66     JNEG <= '1' WHEN (AC_SIGNED(7) = '1') ELSE '0';
67     JPOSZ <= '1' WHEN (JNEG = '0') ELSE '0';
68     JZERO <= '1' WHEN (AC_IN = CLR) ELSE '0';
69     JNZER <= '1' WHEN (AC_IN /= CLR) ELSE '0';
70
71     -- EXECUTING THE INSTRUCTION SET
72     MEM_STORE <= STORE when (OPCODE_REG = x"03") else '0';
73     JUMP <= '1' WHEN (OPCODE_IN = x"10") ELSE '0';
74
75     -- OPCODE AFFECTING Z
76     with OPCODE_REG select
77         Z <= NOP when x"00",
78             LOAD when x"01",
79             LOADI when x"02",
80             CLR when x"04",
81             ADD when x"05",
82             ADDI(7 downto 0) when x"06",
83             SUBT when x"07",
84             SUBTI(7 downto 0) when x"08",
85             NEG when x"09",
86             NOT when x"0A",
87             ANDD when x"0B",
88             ORR when x"0C",
89             XOR when x"0D",
90             SHL when x"0E",
91             SHR when x"0F",
92             NOP when OTHERS;
93
94     -- OPCODE AFFECTING LOAD_PC
95     with OPCODE_REG select
96         PC_LOAD <= JUMP when x"10",
97             JNEG when x"11",
98             JPOSZ when x"12",
99             JZERO when x"13",
100            JNZER when x"14",
101            '0' when OTHERS;
102
103 end behavior;

```

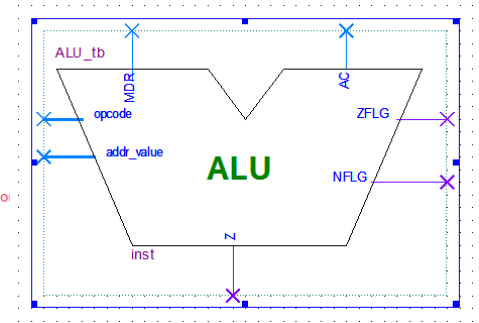


## Fetch

This was a simple multiplexer that chose the PC bus or the ADDR\_VAL bus based on the value of FETCH.

FETCH\_tb.vhd

```
1  -----
2  --EE310 lab 07
3  -- Multiplexer - Fetch
4  --Jessica Atkinson
5  -----
6
7  --importing library
8  library ieee;
9  use ieee.std_logic_1164.all;
10
11 entity fetch_tb is
12     --declaring variable properties
13     port( FETCH : in std_logic;
14           addr_value, pc : in std_logic_vector(7 downto 0);
15           address : out std_logic_vector(7 downto 0));
16 end entity fetch_tb;
17
18 architecture behavior of fetch_tb is
19 begin
20     address <= PC when (FETCH = '1') else addr_value;
21 END behavior;
```

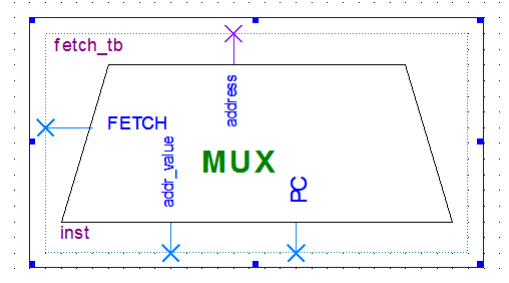


## Instruction Registers

For the instruction registers, initially, I had created one VHDL file that held both the IRL and IRU. For this lab, I took that code and separated it into the following two files to represent the Upper and Lower Instruction register separately.

IRL.vhd

```
1  -----
2  -- EE310 Lab#7
3  -- Jessica Atkinson
4  -- NAU
5  -----
6  -- Instruction Register Lower
7  -----
8
9  --declaring libraries used
10 library ieee;
11 use ieee.std_logic_1164.all;
12 use ieee.numeric_std.all;
13 library altera_mf;
14 use altera_mf.altera_mf_components.all;
15
16 entity IRL8 is
17     port( LOAD_IRL, CLK, RESET : in std_logic;
18           MDR : in std_logic_vector(7 downto 0);
19           ADDR_VALUE : out std_logic_vector(7 downto 0));
20 end IRL8;
21
22 architecture behav of IRL8 is
23 begin
24     process(CLK, LOAD_IRL, MDR, RESET)
25     begin
26         if RESET = '1' then
27             ADDR_VALUE <= x"00";
28             --if CLK on FALLING edge and LOAD_IRU =1 then MDR = OPCODE
29         elsif clk'event AND clk = '0' then
30             if (LOAD_IRL = '1') then
31                 ADDR_VALUE <= MDR;
32             end if;
33         end if;
34     end process;
35 end behav;
```

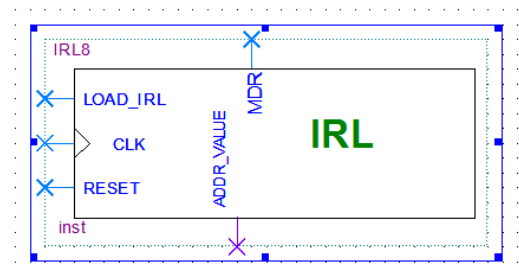


## IRU.vhd

```

3  -- EE310 Lab#7
4  -- Jessica Atkinson
5  -- NAU
6  -- Instruction Register UPPER
7
8  --declaring libraries used
9
10 library ieee;
11 use ieee.std_logic_1164.all;
12 use ieee.numeric_std.all;
13 library altera_mf;
14 use altera_mf.altera_mf_components.all;
15
16 entity IRU8 is
17 port( LOAD_IRU, CLK, RESET : in std_logic;
18       MDR : in std_logic_vector(7 downto 0);
19       OPCODE : out std_logic_vector(7 downto 0));
20 end IRU8;
21
22 architecture behav of IRU8 is
23 begin
24 process(CLK, LOAD_IRU, MDR, RESET)
25 begin
26     if RESET = '1' then
27         OPCODE <= x"00";
28     --if CLK on FALLING edge and LOAD_IRU =1 then MDR = OPCODE
29     elsif (LOAD_IRU = '1') then
30         if clk'event AND clk = '1' then
31             OPCODE <= MDR;
32         end if;
33     end if;
34 end process;
35 end behav;
36
37

```

 

## Program Counter

The program counter increments by one to execute the data stored in the memory location value. This is how the 16-bit data can be stored in four states at which PrepU/L and FetchU/L occur. Storing the upper and lower byte in two separate memory locations in order to store the next bit by incrementing the PC by one.


This is the file I had the most errors with. The code created for the previous lab would only hold x"00" and increment by one to x"01" then back down to x"00" in a loop.

## pc\_tb.vhd

```

1  -- EE310 lab07
2  -- Program Counter
3  -- Jessica Atkinson
4
5  --import libraries
6
7 library ieee;
8 use ieee.std_logic_1164.all;
9 use ieee.numeric_std.all;
10 library altera_mf;
11 use altera_mf.altera_mf_components.all;
12
13 entity pc_tb is
14 --declaring i/o ports
15 port( RESET, clk : in std_logic;
16       addr_value : in std_logic_vector(7 downto 0); --ir_lower
17       LOAD_PC, INCR_PC : in std_logic;
18       --ProgramCounter : out std_logic_vector(7 downto 0)); --pc bus
19       pc_out : out std_logic_vector(7 downto 0)); --pc bus
20 end entity pc_tb;
21
22 architecture behavior of pc_tb is
23 --signal pc_out : std_logic_vector(7 downto 0); -- TMP VARS for increments
24 signal pc_store : std_logic_vector(7 downto 0);
25 begin
26     pc_out <= pc_store;
27     process(clk, RESET, addr_value, INCR_PC, LOAD_PC, pc_store)
28     begin
29         IF RESET = '1' then
30             --IF reset active
31             --pc_out <= "00000000"; --clear register
32             pc_store <= "00000000"; --clear store
33         ELSIF clk'event AND clk = '1' then --ELIF clk rising edge triggered
34             IF LOAD_PC = '1' then --IF LOAD_PC active
35                 --pc_out <= addr_value; --load addr_value
36                 pc_store <= addr_value;
37             ELSIF INCR_PC = '1' then --IF INCR_PC active
38                 --pc_out <= pc_store + 1; --increment + 1 PER KEY0 ACTIVE
39                 pc_store <= std_logic_vector(unsigned(pc_store) + 1);
40             END IF;
41         END IF;
42     end process;
43 end behavior;
44
45

```

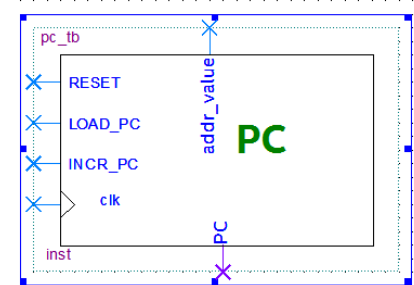

## Activity 2: Control Unit for Instruction Fetch

control\_unit.vhd

### Control Unit

The control unit was straight forward on how to structure the VHDL code. Declaring the state\_types then variables that will indicate what state it is at. While alternating various signals to go off for each state, there is an if statement that will determine if the third bit in the STATE variable is a 1. If it is a one then it returns the states to the start if not it moves to the next. Once reaching the last state, FetchL it will skip the start state unless reset is being pressed and move on to PrepU.

```


1  -----
2  -- EE310 Control Unit
3  -- Created: May 8, 2018
4  -- Creator: Jessica Atkinson
5  -- 5-State Finite State Machine
6  -----
7
8  library ieee;
9  use ieee.std_logic_1164.all;
10
11 entity control_unit is
12     port( NFLG, ZFLG, RESET, CLK : in std_logic;
13           OPCODE : in std_logic_vector(7 downto 0);
14           STATE : BUFFER std_logic_vector(2 downto 0);
15           LOAD_AC, LOAD_IRU, LOAD_IRL, LOAD_PC, INCR_PC, FETCH, MEM_STORE : out std_logic);
16 end control_unit;
17
18 architecture behavior of control_unit is
19     type state_type is (start, PrepU, FetchU, PrepL, FetchL);
20     signal present_state, next_state, LAST_STATE : state_type;
21     signal AC_LOAD, MEM_STORE : STD_LOGIC;
22 begin
23     sync_proc:
24     process(CLK, RESET)
25     begin
26         --
27         if RESET = '1' then
28             present_state <= start;
29         elsif (clk'event and CLK = '0') then
30             present_state <= next_state;
31         end if;
32     end process;
33
34     comb_proc:
35     process(present_state, next_state)
36     begin
37         case present_state is
38             -- start
39             when start =>
40                 next_state <= PrepU;
41                 STATE <= "100";
42                 FETCH <= '0';
43                 LOAD_IRL <= '0';
44                 LOAD_IRU <= '0';
45                 LOAD_AC <= '0';
46                 INCR_PC <= '0';
47             -- PrepU
48             when PrepU =>
49                 STATE <= "000";
50                 FETCH <= '1';
51                 LOAD_IRL <= '0';
52                 INCR_PC <= '0';
53                 LOAD_AC <= '0';
54                 if STATE(1) = '1' then
55                     next_state <= start;
56                 else
57                     next_state <= FetchU;
58                 end if;
59             -- FetchU
60             when FetchU =>
61                 STATE <= "001";
62                 FETCH <= '0';
63                 LOAD_IRU <= '1';
64                 INCR_PC <= '1';
65                 if STATE(1) = '1' then
66                     next_state <= start;
67                 else
68                     next_state <= PrepL;
69                 end if;
70             -- PrepL
71             when PrepL =>
72                 STATE <= "010";
73                 FETCH <= '1';
74                 LOAD_IRU <= '0';
75                 INCR_PC <= '0';
76                 if STATE(2) = '1' then
77                     next_state <= start;
78                 else
79                     next_state <= FetchL;
80                 end if;
81             -- FetchL
82             when FetchL =>
83                 STATE <= "011";
84                 FETCH <= '0';
85                 LOAD_IRL <= '1';
86                 INCR_PC <= '1';
87                 if STATE(2) = '1' then
88                     next_state <= start;
89                 else
90                     next_state <= PrepU;
91                 end if;
92         end case;
93     end process;
94 end behavior;
95

```


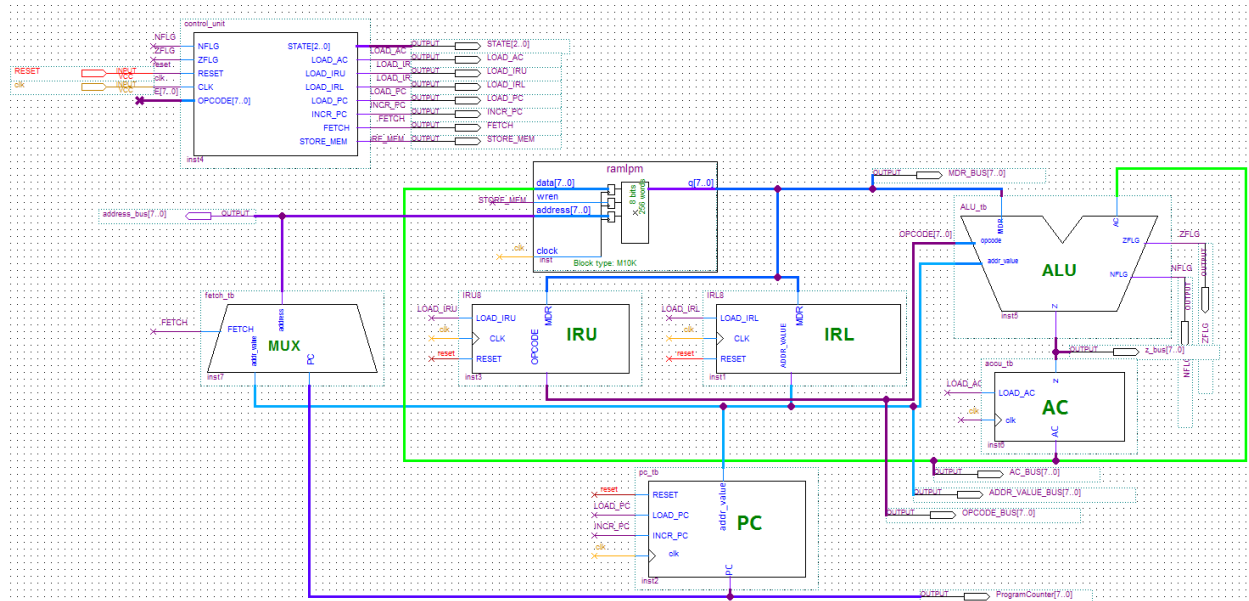
## Block Diagram File

I added the new control box above the original block diagram and labeled the bus lines so they will update accordingly and not have too many wires to follow.



## Force File

The force file didn't have many operations. This is because many of the inputs are coming from a different location and do not need to be set. Therefore the 8-bit OPCODE input comes from the OPCODE\_BUS[7..0]. The ZPLG and NPLG are controlled from the output of the ALU. This leaves the clock and reset as the controls that can be altered in the force file. Therefore, I put the clock in a 100ns cycle alternating from 0 to 1 every 50ns. Setting reset to '1' for the first 25ns and zero for the rest of the simulation.

```
#####
# EE310 Lab07
# Force File
# Demonstrate Control Signals
#####

restart -force


# Reset and clear all registers
force RESET 1 0ns ;
force clk 0 0ns, 1 50ns -r 100ns;

# Set Reset=0 then run
run 25ns;
force RESET 0 0ns;
run 1075ns;
#####//end
```
 
## Waveform

This waveform below shows the STATE values starting at '100' := RESET then it cycles from '000' PrepU to '001' FetchU to '010' PrepL to '011' FetchL. This cycle is set to repeat and only include the 4<sup>th</sup> state if and only if the reset button is being pressed.

The inputs are in green and orange. The outputs include the STATE signal in lime-green and the busses in blue and the NFLG and ZFLG in green at the bottom. For this waveform the iteration limit error (vsim-3601) reached at 1050 ns in the middle of the 11<sup>th</sup> clock cycle during the FetchU state. I have written numerous versions of the force file and all of them stop on the rising edge of the FetchU state.



The table below shows what the signals should be during each state as well as their state value.

	1	2	3	4	5
	Start	PrepU	FetchU	PrepL	FetchL
<b>RESET</b>	1	0	0	0	0
<b>STATE(3)</b>	100	000	001	010	011
<b>LOAD_AC</b>	0	0	0	0	0
<b>LOAD_IRU</b>	0	0	1	0	0
<b>LOAD_IRL</b>	0	0	0	0	1
<b>LOAD_PC</b>	0	0	0	0	0
<b>INCR_PC</b>	0	0	1	0	1
<b>FETCH</b>	0	1	0	1	0
<b>STORE_MEM</b>	0	0	0	0	0

## Conclusion

This lab showed me how to connect the previous labs to make a basic microprocessor. I ran into many issues including having to change the active RESET from '0' to '1' in all the registers as well as changing a few clock edges to activate on the rising edge. My program counter's VHDL has the most issues. Overall, this lab was helpful to realize how each part contributed to the microprocessor and what control lines operate different registers and update different data busses.